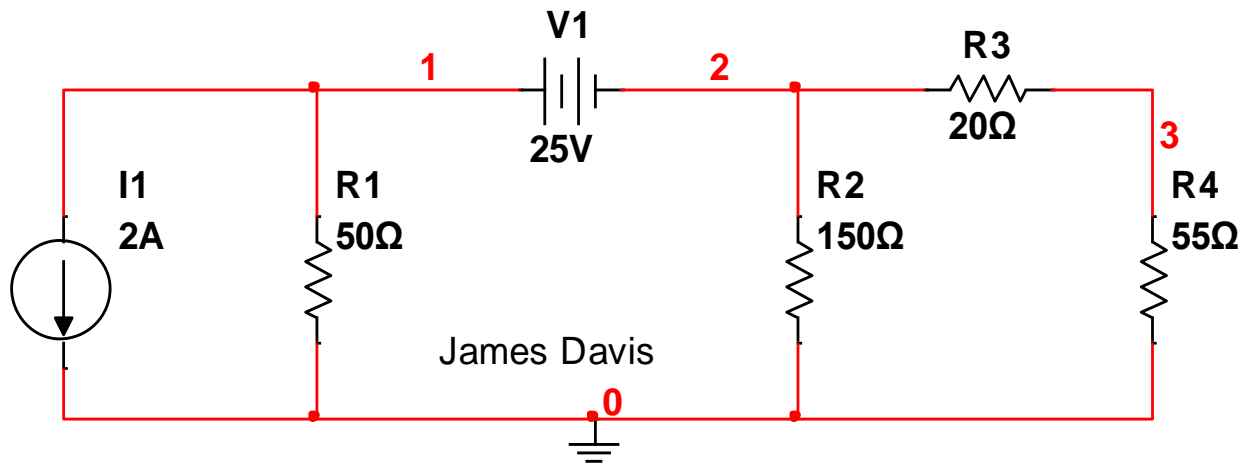
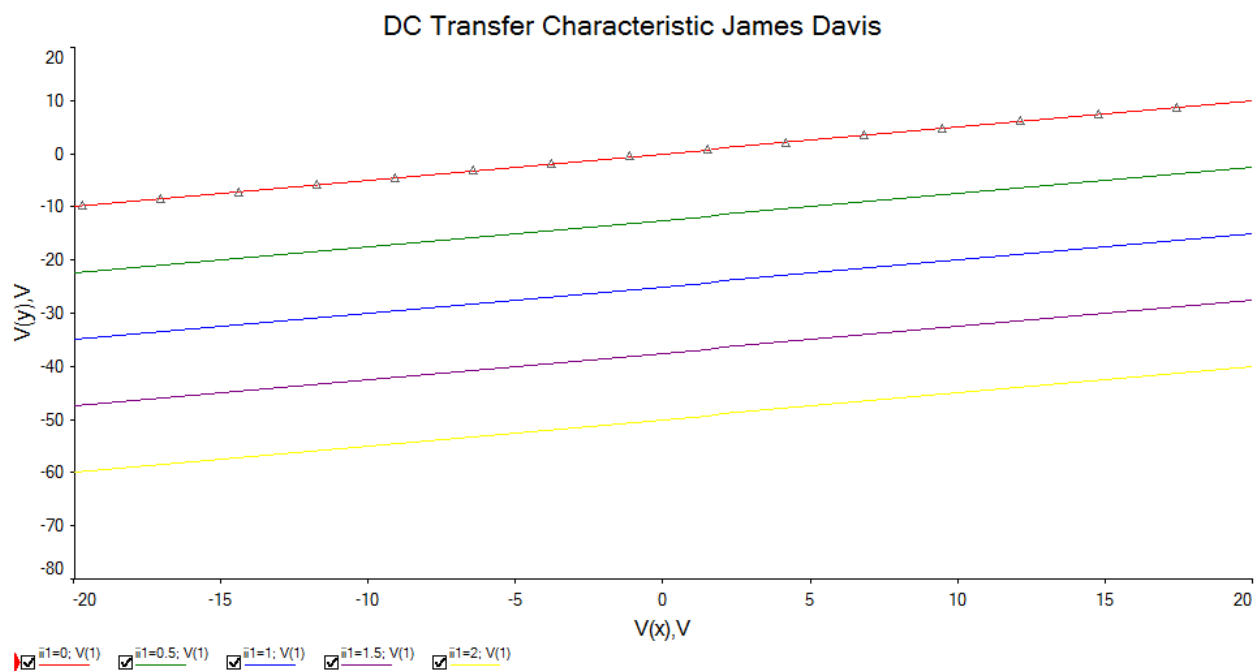


**EGN3204 — Engineering Software Tools**  
**Pensacola (82151) Section, Fall 2014**  
**Problem Set #6 (October 2<sup>nd</sup>, 2014 Lecture)**  
**(Word, Multisim 2013)**

1. The circuit design for problem one is given in Figure 1, while the DC Sweep output for problem one is given in Figure 2.

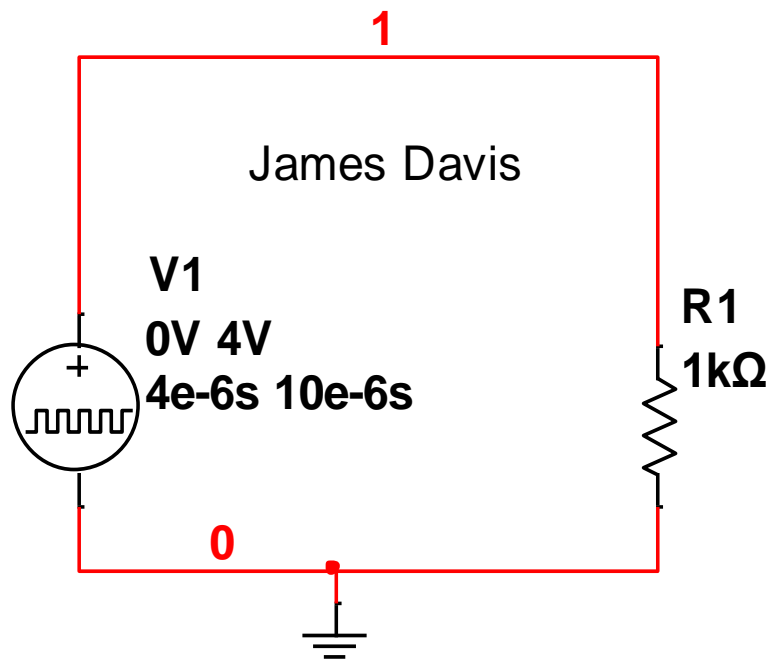


**Figure 1.** The circuit schematic for problem one.

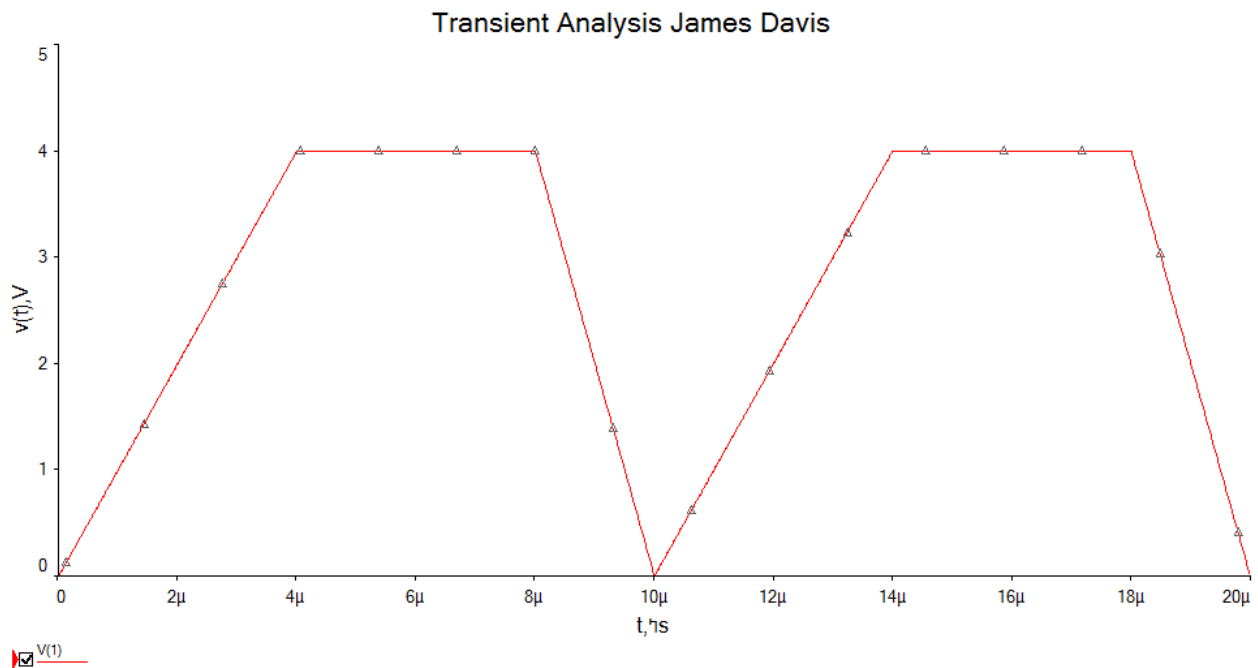


**Figure 2.** The DC Sweep grapher output for problem 1.

2. The circuit schematic for problem two is given in Figure 3, and the grapher output for the Transient Analysis is given in Figure 4.

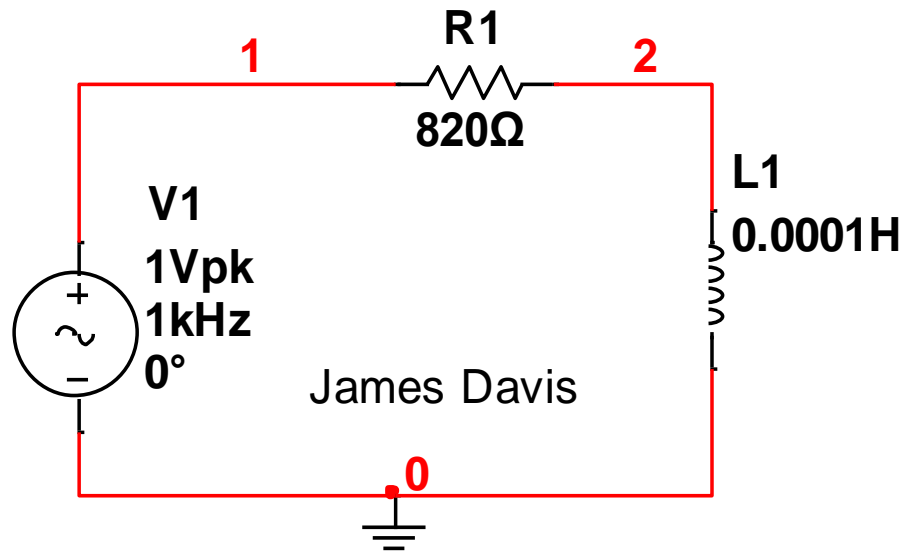


**Figure 3.** Circuit schematic for problem two.

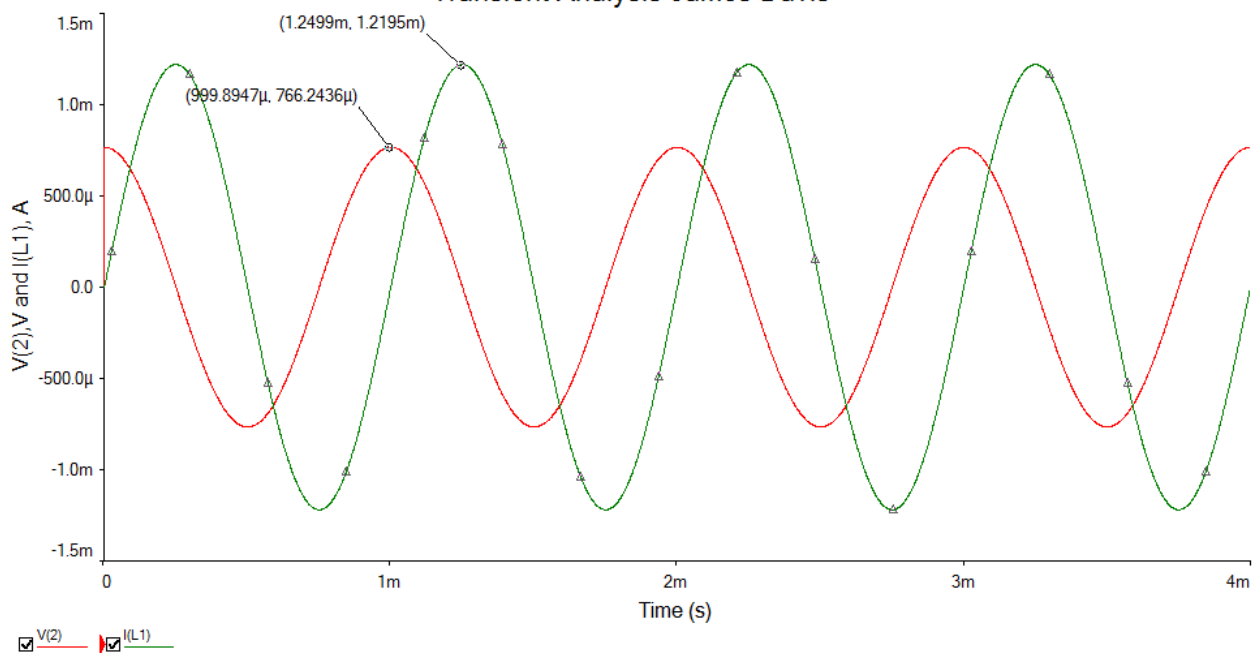


**Figure 4.** Transient analysis output for problem two.

3. The circuit schematic for problem three is given in Figure 5. The Transient Analysis grapher output window is given in Figure 6.



**Figure 5.** The circuit schematic for problem three.  
Transient Analysis James Davis



**Figure 6.** The Transient Analysis grapher output window for problem three.

As can be seen from the grapher output window the time  $t_v = 989.89 \cdot 10^{-6} \text{ s}$  and  $t_i = 1.2499 \cdot 10^{-3} \text{ s}$ .  
Given the equation:

$$\Delta\theta = \frac{|t_v - t_i|}{T} * 360^\circ \text{ where } T \text{ is the period for voltage source.}$$

Then it follow that:  $\Delta\theta = 96^\circ$